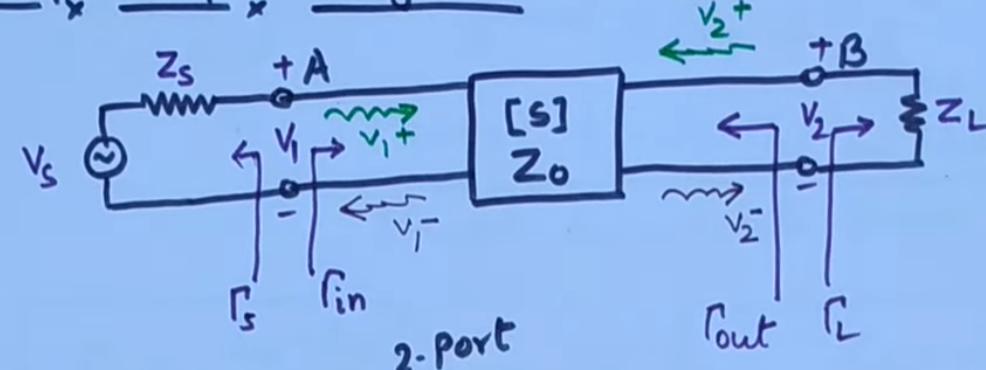


①

Two port power gain

MICROWAVE AMPLIFIER
DESIGN.



Some definitions of power gain

A. Power gain $G = \frac{P_L}{P_{in}} = \frac{\text{Power dissipated in } Z_L}{\text{Power delivered to input of the N/w}}$

B. Available power gain $G = \frac{P_{avv}}{P_{avv}} = \frac{\text{Power available from the N/w}}{\text{Power available from the Source}}$

(1)

C. Transducer power gain = $G_T = \frac{P_L}{P_{av}} \quad \text{Power dissipated to the load}$
 $= \frac{\text{Power available from the source.}}{\text{Power available from the source.}}$

$$\Gamma_S = \frac{Z_S - Z_0}{Z_S + Z_0}$$

and

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

From signal flow graph or analytical method
we can write.

$$\Gamma_{in} = \frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L}$$

$$\Gamma_{out} = \frac{V_2^-}{V_2^+} = S_{22} + \frac{S_{12} S_{21} \Gamma_S}{1 - S_{11} \Gamma_S}$$

NOTE
 $V_1^- = S_{11} V_1^+ + S_{12} V_2^+$
 $= S_{11} V_1^+ + S_{12} \Gamma_L V_2^-$
and $(\because \Gamma_L = \frac{V_2^+}{V_2^-})$

$$V_2^- = S_{21} V_1^+ + S_{22} V_2^+$$
 $= S_{21} V_1^+ + S_{22} \Gamma_L V_2^-$

(3)

$$v_2^- = S_{21} v_1^+ + S_{22} r_L v_2^-$$

$$\Rightarrow v_2^- (1 - S_{22} r_L) = S_{21} v_1^+ \text{ i.e. } v_2^- = \left(\frac{S_{21}}{1 - S_{22} r_L} \right) v_1^+$$

Apply voltage division at A:

$$v_1^- = v_s \left(\frac{Z_{in}}{Z_s + Z_{in}} \right) \Rightarrow (v_1^+ + v_1^-) = v_s \left(\frac{Z_{in}}{Z_s + Z_{in}} \right)$$

$$(v_1^+ + r_{in} v_1^+) = v_s \frac{Z_0 \left(\frac{1 + r_{in}}{1 - r_{in}} \right)}{Z_0 \left(\frac{1 + r_s}{1 - r_s} + \frac{1 + r_{in}}{1 - r_{in}} \right)}$$

[All impedance
in reflection
coefficient]

$$v_1^+ \left(\frac{1 + r_{in}}{1 - r_{in}} \right) = v_s \left(\frac{1 + r_{in}}{1 - r_{in}} \right) \left(\frac{(1 - r_s)(1 - r_{in})}{1 + r_s - r_{in} - r_s r_{in} + 1 - r_s + r_{in} - r_{in} r_s} \right)$$

$$v_1^+ = v_s \left(\frac{1 - r_s}{2 \left(1 - r_s r_{in} \right)} \right)$$



7:50 / 20:35

Scroll for details



(4)

Avg. Power delivered to the network (P_{in})

$$\rightarrow P_{in} = \frac{|V_1^+|^2}{2Z_0} (1 - |\Gamma_{in}|^2)$$

$$P_{in} = \frac{|V_s|^2 |1 - \Gamma_s|^2}{8Z_0 |1 - \Gamma_s \Gamma_{in}|^2} (1 - |\Gamma_{in}|^2)$$

→ Power delivered to the load

$$P_L = \frac{|V_2^-|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

$$= \left| \frac{S_{21} V_1^+}{1 - S_{22} \Gamma_L} \right|^2 \cdot \frac{1}{2Z_0} (1 - |\Gamma_L|^2)$$

$$\therefore V_2^- = \frac{S_{21} V_1^+}{1 - S_{22} \Gamma_L}$$

(5)

$$P_L = \frac{|V_s|^2}{8Z_0} \frac{(1-|r_L|^2) |(1-r_s)^2 |S_{21}|^2}{|(1-S_{22}r_L)|^2 |(1-r_s r_{in})|^2}$$

i.e. Power gain (G) = $\frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1-|r_L|^2)}{(1-|r_{in}|^2) |(1-S_{22}r_L)|^2}$

Power available from the source.

$$P_{avS} = P_{in}|_{max} = P_{in}|_{r_{in}=r_s^*}$$

$$= \frac{|V_s|^2 |(1-r_s)^2 (1-|r_s|^2)}{8Z_0 |(1-|r_s|^2)|^2} = \frac{|V_s|^2}{8Z_0} \frac{|(1-r_s)|^2}{(1-|r_s|^2)}$$

So,

$$P_{avS} = \frac{|V_s|^2}{8Z_0} \frac{|(1-r_s)|^2}{(1-|r_s|^2)}$$

⑥ Power available from the network

$$P_{\text{avN}} = P_L \left| \frac{|V_s|^2 |S_{21}|^2 (1 - |\Gamma_{\text{out}}|^2) |1 - \Gamma_s|^2}{8Z_0 \cdot |1 - S_{22} \Gamma_{\text{out}}|^2 |1 - \Gamma_s \Gamma_{\text{in}}|^2} \right.$$

$$\left. \left| \frac{|1 - \Gamma_s \Gamma_{\text{in}}|^2}{\Gamma_L = \Gamma_{\text{out}}} \right. \right| = \frac{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{\text{out}}|^2)^2}{|1 - S_{22} \Gamma_{\text{out}}|^2} \checkmark$$

$$P_{\text{avN}} = \frac{|V_s|^2}{8Z_0} \frac{|S_{21}|^2 |1 - \Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{\text{out}}|^2)}$$

$$\boxed{\text{Available power gain } (G_A) = \frac{P_{\text{avN}}}{P_{\text{avS}}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{|1 - S_{11} \Gamma_s|^2 (1 - |\Gamma_{\text{out}}|^2)}}$$

$$\boxed{\text{Inducer power gain } (G_I) = \frac{P_L}{P_{\text{avS}}} = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)^2 (1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{\text{in}}|^2 |1 - S_{22} \Gamma_L|^2}}$$



16:16 / 20:35

Scroll for details



7

gf

$\Gamma_L = 0$ & $\Gamma_S = 0$ (i.e. Input and output are matched for zero reflection coefficient).

$$G_T = |S_{21}|^2$$

Unilateral transducer power gain (G_{TU})

if $S_{12} = 0$, $\Gamma_{in} = S_{11}$ and $\Gamma_{out} = S_{22}$

$$G_{TU} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|(1 - S_{11}\Gamma_S)|^2 |(1 - S_{22}\Gamma_L)|^2}$$

G_T as separate components

$$G_T = \left(\frac{1 - |\Gamma_S|^2}{|1 - \Gamma_{in}\Gamma_S|^2} \right) \cdot \left(|S_{21}|^2 \right) \cdot \left(\frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} \right)$$

\downarrow \downarrow \downarrow
 G_S G_0 G_L



18:50 / 20:35

Scroll for details

