

Problem: -

1.1 The S Parameter of the two port network is given. Find whether the network is reciprocal and lossless.

$$S = \begin{bmatrix} 0.2 + j0.4 & 0.8 - j0.4 \\ 0.8 - j0.4 & 0.2 + j0.4 \end{bmatrix}$$

Solution:-

(i) $[S] = [S]^T$ for Reciprocal NW

(OR)

$$S_{ij} = S_{ji} \text{ i.e.,}$$

$$[S]^T = \begin{bmatrix} 0.2 + j0.4 & 0.8 - j0.4 \\ 0.8 - j0.4 & 0.2 + j0.4 \end{bmatrix}$$

$$\Rightarrow [S] \quad S_{12} = S_{21} \text{ etc.}$$

Given network is Reciprocal.

(ii) $[S]^* [S]^T = U$ for lossless NW

(OR) $S_{11}S_{11}^* + S_{12}S_{12}^* = 1$ or

$$|S_{11}|^2 + |S_{12}|^2 = 1$$

$$(0.04 + 0.16) + (0.64 + 0.16) = 1$$

$$1 = 1$$

Condition is Satisfied

$$U = \begin{bmatrix} 0.2 + j0.4 & 0.8 - j0.4 \\ 0.8 - j0.4 & 0.2 + j0.4 \end{bmatrix} \begin{bmatrix} 0.2 - j0.4 & 0.8 + j0.4 \\ 0.8 + j0.4 & 0.2 - j0.4 \end{bmatrix}$$

$$= \begin{bmatrix} 0.04 + 0.16 + 0.64 + 0.16 & 0.16 - 0.16 + 0.16 - 0.16 \\ 0.16 - 0.16 + 0.16 - 0.16 & 0.64 + 0.16 + 0.04 + 0.16 \end{bmatrix}$$

$$U = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

condition is satisfied,

Given Network is Lossless.

2020/8/27 14:07

1.2) 'S' parameter of a two port network is given by $S_{11} = 0.2 \angle 0^\circ$, $S_{22} = 0.1 \angle 0^\circ$, $S_{12} = 0.6 \angle 90^\circ$ & $S_{21} = 0.6 \angle 0^\circ$. (1) Prove that Network is reciprocal but not lossless. (2) Find the return loss at port 1 when port 2 is short circuit.

Solution:-

$$(1) [S] = \begin{bmatrix} 0.2 \angle 0^\circ & 0.6 \angle 90^\circ \\ 0.6 \angle 90^\circ & 0.1 \angle 0^\circ \end{bmatrix}$$

For reciprocal N/w, $S_{ij} = S_{ji}$ $\therefore S_{12} = S_{21} = 0.6 \angle 90^\circ$

both are same. \therefore This is reciprocal Network (OR)
 $[S] = [S]^T$, which also true for above matrix.

For lossless Network,

$$S_{11} S_{11}^* + S_{12} S_{12}^* = 1$$

$$|S_{11}|^2 + |S_{12}|^2 = 1$$

$$(0.2)^2 + (0.6)^2 = 1$$

$$0.04 + 0.36 = 1$$

$$\Rightarrow 0.4 < 1$$

\therefore The network is ^{not} lossless.

$[S]^* [S]^T = [0]$ also not applicable.

(2) The input reflection coefficient for mismatched load

is given as,

$$\Gamma_1 = S_{11} + \frac{S_{12}^2 \Gamma_2}{1 - S_{22} \Gamma_2}$$

If port 2 is short circuited, so that $T_2 = -1$, then

$$T_1 = S_{11} + \frac{S_{12}^2 (-1)}{1 - S_{22} (-1)}$$

Substitute S_{11} , S_{12} and S_{22} ,

$$T_1 = 0.2 + \frac{(0.5 \angle 90^\circ)^2 (-1)}{1 - (0.1) (-1)}$$

$$T_1 = 0.2 + \frac{(-0.36) (-1)}{1 + 0.1}$$

$$T_1 = 0.2 + \frac{0.36}{1.1} = 0.2 + 0.3273$$

$$T_1 = 0.5273$$

$$\begin{aligned} \text{Return Loss (dB)} &= 20 \log \left(\frac{1}{T_1} \right) \\ &= 20 \times \log \left(\frac{1}{0.5273} \right) \end{aligned}$$

$$\text{Return loss (dB)} = 5.56 \text{ dB}$$

1.3) The S parameters of a port N/w are given by $S_{11} = 0.2 \angle 90^\circ$, $S_{12} = 0.5 \angle 90^\circ$, $S_{22} = 0.2 \angle 90^\circ$, $S_{21} = 0.5 \angle 0^\circ$.

(1) Determine whether the network is lossy or not.

(2) Is the Network symmetrical and reciprocal find the insertion loss of the Network.

Solution:-

$$[S] = \begin{bmatrix} 0.2 \angle 90^\circ & 0.5 \angle 90^\circ \\ 0.5 \angle 0^\circ & 0.2 \angle 90^\circ \end{bmatrix}$$

For lossless,

$$S_{11} \cdot S_{11}^* + S_{12} \cdot S_{12}^* = 1$$

$$|S_{11}|^2 + |S_{12}|^2 = 1$$

$$(0.2)^2 + (0.5)^2 = 1$$

$$0.04 + 0.25 = 1$$

$$0.29 = 1 \Rightarrow \underline{0.29 < 1}$$

\therefore The network is not lossless,

For Reciprocal Networks

$$S_{ij} = S_{ji}$$

$$S_{12} = S_{21}$$

$$0.5 \angle 90^\circ = 0.5 \angle 0^\circ$$

The angle is not same. \therefore it is not symmetrical.

Insertion Loss (dB) :-

$$= 20 \cdot \log \cdot \frac{1}{|S_{21}|}$$

$$= 20 \cdot \log \cdot \frac{1}{|S_{21}|}$$

$$= 20 \cdot \log \cdot \frac{1}{(0.5)(1)}$$

$$= 20 \times \log \frac{1}{(0.5)}$$

$$\boxed{IL = 6.02 \text{ dB}}$$

Q.4) A four port Network has the following Matrix

$$[S] = \begin{bmatrix} 0.1 \angle 90^\circ & 0.6 \angle -45^\circ & 0.6 \angle 45^\circ & 0 \\ 0.6 \angle -45^\circ & 0 & 0 & 0.6 \angle 45^\circ \\ 0.6 \angle 45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.6 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}$$

1.5) A four port network has the following,

$$[S] = \begin{bmatrix} 0.1 \angle 90^\circ & 0.8 \angle -45^\circ & 0.3 \angle 45^\circ & 0 \\ 0.8 \angle -45^\circ & 0 & 0 & 0.4 \angle 45^\circ \\ 0.3 \angle 45^\circ & 0 & 0 & 0.6 \angle -45^\circ \\ 0 & 0.4 \angle 45^\circ & 0.6 \angle -45^\circ & 0 \end{bmatrix}$$

1. Is the Network is lossless 2. Is the NW is reciprocal
- (3). Find the return loss at port 1 when all other ports are terminated with the matched load. (4). What is insertion loss b/w port 2 and port 4 when all other ports are terminated with matched load.
- 5) What is the reflection Co-efficient seen at port 1 when short circuit is placed at port 3 and all other ports are terminated with the matched load.

Solution:-

(1) For lossless NW,

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1$$

$$(0.1)^2 + (0.8)^2 + (0.3)^2 + 0 = 1$$

$$0.01 + 0.64 + 0.09 + 0 = 1$$

$$0.74 < 1$$

The network is not lossless

(2) For Reciprocal,

$$S_{ij} = S_{ji}$$

$$S_{12} = S_{21} = 0.8 \angle -45^\circ \quad ; \quad S_{23} = S_{32} = 0$$

The network is Reciprocal.

- 1) Is the Network is lossless 2) Is the Network is reciprocal
 3) What is the return loss at port 1 and all other ports are matched,

Solution:-

1. Lossless:-

$$\sum_{i=1}^N S_{ij} S_{ij}^* = 1$$

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = 1$$

$$(0.1)^2 + (0.6)^2 + (0.6)^2 + (0)^2 = 1$$

$$0.01 + 0.36 + 0.36 = 1$$

$$0.73 = 1 \Rightarrow \text{Not true, because } 0.73 < 1$$

The network is ~~lossless~~. Not lossless

2. Reciprocal :-

$$S_{ij} = S_{ji} \quad (\text{or}) \quad [S] = [S]^T$$

$$S_{12} = S_{21} \quad \text{or} \quad S_{13} = S_{31} \quad \text{or} \quad S_{41} = S_{14}$$

All conditions are true here. the network is reciprocal.

3. If all the ports are Matched ,

* Given is a four port NW, then $a_2, a_3, a_4 = 0$,

So that $T_2 = 0, T_3 = 0, T_4 = 0$.

$$b_1 = S_{11} a_1 + S_{12} a_2 + S_{13} a_3 + S_{14} a_4$$

$$\therefore S_{11} = \frac{b_1}{a_1} = 0.1 \angle 90^\circ$$

$$\therefore T_1 = 0.1$$

Return Loss (dB) \Rightarrow

$$RL = 20 \log \frac{1}{T_1}$$

$$= 20 \log \frac{1}{0.1}$$

$$RL = 20 \text{ dB}$$

(3) Return loss

$$RL = 20 \log \frac{1}{\Gamma_1}$$

$$\Gamma_1 = |S_{11}| = \left| \frac{b_1}{a_1} \right|$$

Here

$$b_1 = S_{11}a_1 + S_{12}a_2 + S_{13}a_3 + S_{14}a_4$$

P_2, P_3, P_4 are matched, so that $a_2, a_3, a_4 = 0$

$$b_1 = S_{11}a_1 \Rightarrow S_{11} = 0.1 \angle 90^\circ$$

$$\Gamma = 0.1$$

$$\begin{aligned} \text{Return loss (dB)} &= 20 \log \frac{1}{\Gamma_1} \\ &= 20 \log \frac{1}{0.1} \end{aligned}$$

$$\boxed{RL = 20 \text{ dB}}$$

(4) Insertion loss b/w Port 2 and Port 4.

$$\begin{aligned} IL &= 20 \log \frac{1}{|S_{24}|} \\ &= 20 \times \log \frac{1}{|0.41|} \end{aligned}$$

$$\boxed{IL = 7.95 \text{ dB}}$$

(5) Reflection Coefficient :-

Here port 3 is short circ'd, $\Gamma_3 = -1$

At Port 1,

$$\Gamma_1 = S_{11} + \frac{S_{13}^2 \Gamma_3}{1 - S_{33} \Gamma_3} \Rightarrow \frac{0.1 \angle 90^\circ + (0.3 \angle 45^\circ)^2 (-1)}{1 - 0}$$

$$= 0.1 \angle 90^\circ + \frac{(0.3 \angle 45^\circ)^2 (-1)}{1 - 0}$$

$$= 0.1 \angle 90^\circ + (0.3 \angle 45^\circ)^2 (-1)$$

$$= 0.1 \angle 90^\circ + 0.09 \angle 180^\circ$$

$$\Gamma_1 = 0.1j + 0.09j = -0.19j //$$

$$\boxed{\Gamma_1 = -0.19j}$$

1.6. A 5dB attenuator is having VSWR of 1.2 assuming the device is reciprocal. Find S' parameter.

Solution:-

$$S = 1.2$$

$$\Gamma = \frac{S-1}{S+1} \Rightarrow \Gamma = \frac{1.2-1}{1.2+1} = \frac{0.2}{2.2}$$

$$\boxed{\Gamma = 0.09}$$

For matched networks, there is no i/p or o/p at Port 2, $a_2 = 0$

$$S_{11} = S_{22} = 0.09$$

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_1 = S_{11} a_1$$

Also, $b_2 = a_1 + b_1$

$$b_2 = a_1 + S_{11} \cdot a_1$$

$$b_2 = a_1 (1 + S_{11})$$

$$\frac{b_2}{a_1} = S_{21} = 1 + S_{11}$$

$$= 1 + 0.09$$

$$\boxed{S_{21} = 1.09}$$

$$\boxed{S_{12} = S_{21} = 1.09}$$

$$b_1 = S_{11} a_1 + S_{12} a_2$$

$$b_2 = S_{21} a_1 + S_{22} a_2$$

$$b_1 = S_{11} \cdot a_1 \Rightarrow \boxed{b_1 = 0.09 a_1}$$

$$b_2 = S_{21} a_1$$

$$b_1 = 0.09 \cdot (b_2 / S_{21})$$

?

1.7. An input of an amplifier has VSWR of 2 and output has VSWR of 3. Find S' parameters, S_{11} , S_{12} under matched condition.

Solution:-

$$S = 2$$

$$\Gamma_{1/p} = \frac{S-1}{S+1}$$

$$\Gamma_{1/p} = 0.33$$

or
 $\Gamma_1 = 0.33$

$$S = 3$$

$$\Gamma_{o/p} = \frac{S-1}{S+1}$$

$$\Gamma_{o/p} = 0.5$$

or

$$\Gamma_2 = 0.5$$

7. In a waveguide termination having VSWR of 1.1 is used to dissipate 100 Watts of power. Find the reflected Power P_r

Sol:-

$$T = \frac{S-1}{S+1} = \frac{1.1-1}{1.1+1} = \frac{0.1}{2.1} = 0.04762$$


$$|T|^2 = \frac{P_r}{P_{in}}$$

$$P_r = |T|^2 \cdot P_{in}$$

$$= (0.04762)^2 \times 100$$

$$P_r = 0.2268 \text{ Watts}$$

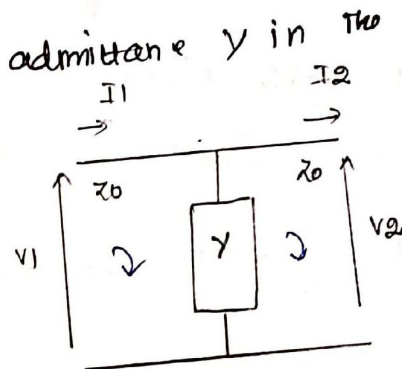8. Find ABCD parameters of the shunt admittance Y in the transmission line shown in figure.



Solution:-

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2 \rightarrow (1)$$

$$I_1 = CV_2 - DI_2 \rightarrow (2)$$

In a given Network, apply mesh analysis

$$V_1 = I_1 Y - I_2 Y \quad ; \quad V_2 = I_1 Y - I_2 Y$$

$$\text{Here } V_1 = V_2 \rightarrow (3) \quad [\text{parallel network}]$$

$$A = \frac{V_1}{V_2} = 1 \Big|_{I_2=0} \quad ; \quad \text{and } B = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

$$C = -\frac{I_1}{V_2} = ? \Big|_{V_2=0} \quad ; \quad D = \frac{I_1}{I_2} \Big|_{V_2=0}$$

While P_2 is shorted $V_2=0$, then $V_1=0$,

$$B=0$$

When P_2 open ckted $I_2=0$,


$$V_1 = I_1 Y$$

$$V_2 = \frac{I_1 - I_2}{Y} \quad , \text{ ie)$$

$$I_1 = V_2 Y + I_2 \quad - (4) \quad , \text{ compare (4) with (2)}$$

$$C = Y, D = 1$$

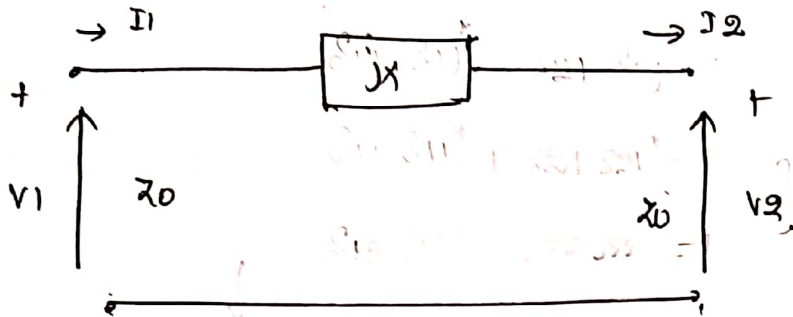1.9 Find the ABCD parameters of the series reactance jX placed in the following transmission line.



Solution:-

Here $I_1 = I_2$, series network,

$$V_1 = AV_2 + BI_2$$

$$I_1 = CV_2 + DI_2$$

$$\therefore \boxed{D = I} \quad , \quad C = \frac{I_1}{V_2} \quad | \quad I_2 = 0, \quad \boxed{C = 0}$$

$$A = \frac{V_1}{V_2} \quad | \quad I_2 = 0, \quad B = \frac{V_1}{I_2} \quad | \quad V_2 = 0.$$


Here
$$I_2 = \frac{V_1 - V_2}{jX} \Rightarrow V_1 = I_2(jX) + V_2$$

$$A = 1 \quad B = jX$$

$$ABCD = \begin{bmatrix} 1 & jX \\ 0 & 1 \end{bmatrix}$$

1.10. In a lossless transmission line of characteristic impedance Z_0 , a series reactance jX and two shunt susceptances jB are placed as shown in figure. Find the ABCD parameters for the network.

Solution:-

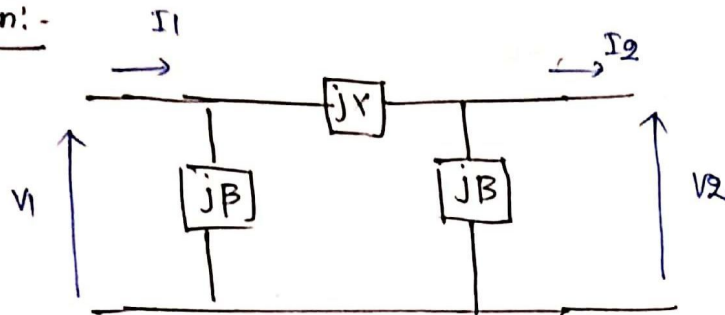


Here the network is symmetric & cascaded.

$$[ABCD] = [ABCD]_1 + [ABCD]_2 + [ABCD]_3$$

$$= \begin{bmatrix} 1 & 0 \\ jB & 1 \end{bmatrix} \begin{bmatrix} 1 & jX \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ jB & 1 \end{bmatrix}$$

$$[ABCD] = \begin{bmatrix} 1 - BX & jX \\ jB(2 - BX) & (1 - BX) \end{bmatrix}$$

1.11 Find ABCD parameters.

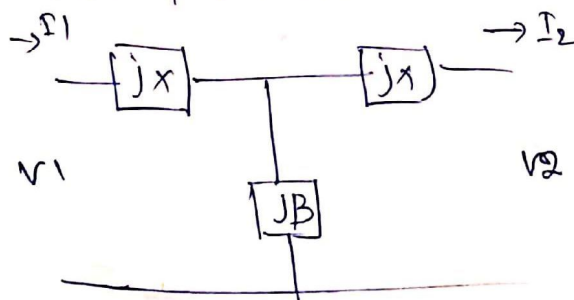

$$[ABCD] = \begin{bmatrix} 1 & jX \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ jB & 1 \end{bmatrix} \begin{bmatrix} 1 & jX \\ 0 & 1 \end{bmatrix}$$

$$[ABCD] = \begin{bmatrix} 1 - BX & jX(2 - BX) \\ jB & 1 - BX \end{bmatrix}$$