

UNIT V RF AMPLIFIER DESIGN AND MATCHING NETWORKS

16ECT72-RF and Microwave Engineering

UNIT V RF AMPLIFIER DESIGN AND MATCHING NETWORKS

Course Handling Faculty

Ms.S.Thilagavathi


Assistant Professor

ECE Department

Dr Mahalingam College of Engineering And Technology

Pollachi-03

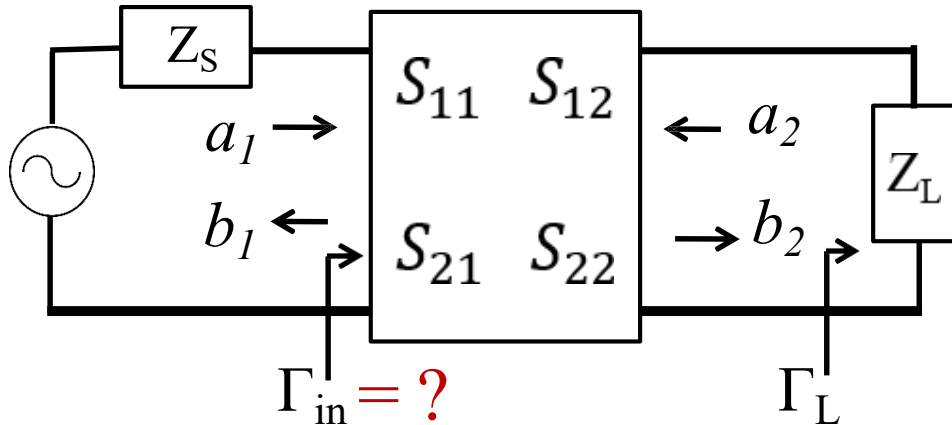Derivation of Γ_{in} of a Device (Amplifier)



$$\Gamma_L = \frac{a_2}{b_2} \Rightarrow a_2 = \Gamma_L b_2 \quad \text{--- (3)}$$

From (1), using (3) & (4)

$$\Gamma_{in} = \frac{b_1}{a_1} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$$



S-Parameters:

$$b_1 = S_{11}a_1 + S_{12}a_2 \quad \text{--- (1)}$$


$$b_2 = S_{21}a_1 + S_{22}a_2 \quad \text{--- (2)}$$

$$b_2 = S_{21}a_1 + S_{22}\Gamma_L b_2$$

$$b_2 = \frac{S_{21}a_1}{1 - S_{22}\Gamma_L} \quad \text{--- (4)}$$

where $\Delta = S_{11}S_{22} - S_{12}S_{21}$

Derivation of Γ_{out} of a Device

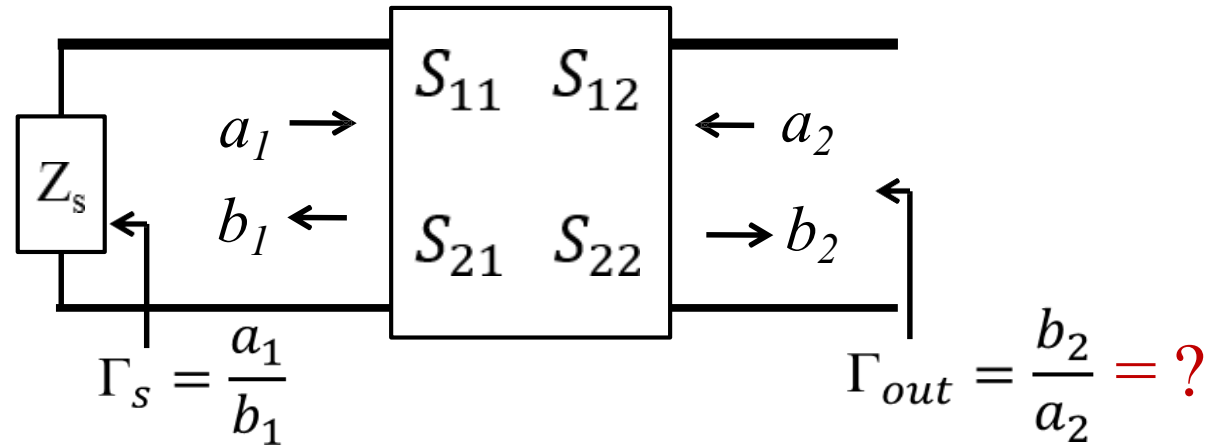

S-Parameters:

$$b_1 = S_{11}a_1 + S_{12}a_2$$

$$b_2 = S_{21}a_1 + S_{22}a_2$$

$$\Gamma_s = \frac{a_1}{b_1} \Rightarrow a_1 = \Gamma_s b_1$$

$$b_1 = S_{11}\Gamma_s b_1 + S_{12}a_2 \longrightarrow b_1 = \frac{S_{12}a_2}{1 - S_{11}\Gamma_s}$$

$$\Gamma_{out} = \frac{b_2}{a_2} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s}$$



$$\Gamma_{out} = \frac{S_{22} - \Delta\Gamma_s}{1 - S_{11}\Gamma_s}$$

Power Gain of an Amplifier

Power Gain	Symbol	Formula
Transducer Power Gain	G_t	$\frac{P_l}{P_{avs}}$
Available Power Gain	G_a	$\frac{P_{avn}}{P_{avs}}$
Operating Power Gain	G_p	$\frac{P_l}{P_{in}}$

P_{in} = Input power

P_l = Power delivered to the load

P_{avs} = Power available from source
 $= P_{in}$, when $\Gamma_{in} = \Gamma_s^*$

P_{avn} = Power available from network
 $= P_l$, when $\Gamma_L = \Gamma_{out}^*$

Power Gain of an Amplifier (contd.)

Transducer Power Gain:

$$G_t = \frac{P_l}{P_{avs}}$$

$$\begin{aligned} P_l &= \frac{1}{2} (|b_2|^2 - |a_2|^2) \\ &= \frac{1}{2} |b_2|^2 (1 - |\Gamma_L|^2) \end{aligned}$$

$$P_{avs} = \frac{\frac{1}{2} |b_s|^2}{1 - |\Gamma_s|^2}$$

$$P_{avs} = \frac{1}{2} |b_s|^2, \text{ if } |\Gamma_s| = 0$$

$$G_t = \frac{1 - |\Gamma_s|^2}{|1 - \Gamma_{in} \Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22} \Gamma_L|^2}$$

$$G_t = \frac{1 - |\Gamma_s|^2}{|1 - S_{11} \Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out} \Gamma_L|^2}$$

Three Cases of Amplifier Gain

Case 1: Matched Transducer Power Gain (G_{tm})

Both input and output ports are matched $\Gamma_s = 0$ $\Gamma_L = 0$ $G_t \rightarrow \boxed{G_{tm} = |S_{21}|^2}$

Case 2: Unilateral Transducer Power Gain (G_{tu})

$|S_{12}| = 0$, Power flow in one direction

$$\boxed{G_{tu} = \frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}}$$

Case 3: Max. Uni. Transducer Power Gain ($G_{tu \max}$)

$\Gamma_s = S_{11}^*$ & $\Gamma_L = S_{22}^*$ \rightarrow Maximum Gain

$$\boxed{G_{tu \max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}}$$

Stability of an Amplifier

1. Unilateral case: $S_{12} = 0 \rightarrow$ Unconditionally Stable

$$\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = S_{11} \quad \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} = S_{22}$$

2. Bilateral case: $S_{12} \neq 0 \rightarrow$ Check Stability of the amplifier

Stability Factor (K):

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2 |S_{12}S_{21}|}$$

$|\Delta| < 1$
&
 $K > 1 \rightarrow$ Amplifier is unconditionally stable

Derivation of Stability Circles

Unconditional Stability \longrightarrow

$$|\Gamma_{out}| \leq 1$$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s} = \frac{S_{22} - \Delta\Gamma_s}{1 - S_{11}\Gamma_s} \longrightarrow |\Gamma_{out}| = 1 \longrightarrow \left| \frac{S_{22} - \Delta\Gamma_s}{1 - S_{11}\Gamma_s} \right| = 1$$

$$(S_{22} - \Delta\Gamma_s)(S_{22} - \Delta\Gamma_s)^* = (1 - S_{11}\Gamma_s)(1 - S_{11}\Gamma_s)^*$$

$$|S_{22}|^2 - S_{22}\Delta^*\Gamma_s^* - \Delta\Gamma_s S_{22}^* + |\Delta|^2|\Gamma_s|^2 = 1 - S_{11}\Gamma_s - S_{11}^*\Gamma_s^* + |S_{11}|^2|\Gamma_s|^2$$

$$|\Gamma_s|^2(|S_{11}|^2 - |\Delta|^2) - \Gamma_s(S_{11} - \Delta S_{22}^*) - \Gamma_s^*(S_{11}^* - \Delta^* S_{22}) + (1 - |S_{22}|^2) = 0$$

Derivation of Stability Circles (contd.)

Equation of a circle: $|\Gamma_s - c_s|^2 = r_s^2$ $c_s \rightarrow \text{Center}$, $r_s \rightarrow \text{Radius}$

$$(\Gamma_s - c_s)(\Gamma_s - c_s)^* = r_s^2 \Rightarrow |\Gamma_s|^2 - \Gamma_s c_s^* - c_s \Gamma_s^* + |c_s|^2 = r_s^2 \quad \text{--- 2}$$

From eq. 1, dividing by $(|S_{11}|^2 - |\Delta|^2)$,

$$|\Gamma_s|^2 - \Gamma_s \frac{(S_{11} - \Delta S_{22}^*)}{|S_{11}|^2 - |\Delta|^2} - \Gamma_s^* \frac{(S_{11}^* - \Delta^* S_{22})}{|S_{11}|^2 - |\Delta|^2} + \frac{(1 - |S_{22}|^2)}{|S_{11}|^2 - |\Delta|^2} = 0 \quad \text{--- 3}$$

Comparing 2 & 3

$$c_s = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad r_s = \left| \frac{S_{12} S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

Stability circle center and radius for Source

Derivation of Stability Circles (contd.)

Equation of a circle for Load:

$$\underline{|\Gamma_L - c_l|^2 = r_l^2} \quad c_l \rightarrow \text{Center}, r_l \rightarrow \text{Radius}$$

By symmetry:

$$c_l = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad r_l = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

Stability circle center
and radius for Load

Amplifier Stability Example

S-parameters of a transistor at 800 MHz are given. Determine the stability of the transistor and plot stability circles on Smith chart.

$$S_{11} = 0.65 \angle -95^\circ$$

$$S_{12} = 0.035 \angle 40^\circ$$

$$S_{21} = 5 \angle 115^\circ$$

$$S_{22} = 0.8 \angle -35^\circ$$

Find K and Δ for Stability Test

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 0.504 \angle 249.6^\circ \rightarrow$$

$$|\Delta| < 1$$

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2 |S_{12}S_{21}|} = 0.547 > 1$$

Transistor is
conditionally stable
at 800 MHz

Stable region on Smith chart needs to be located to choose Γ_s and Γ_L

Amplifier Stability Example (Contd.)

Input (Source) stability circle:


$$c_s = 1.79 \angle 122^\circ, \quad r_s = 1.04$$

Output (Load) stability circle:

$$c_l = 1.3 \angle 48^\circ, \quad r_l = 0.45$$

Unstable region for Γ_s

Unstable region for Γ_L

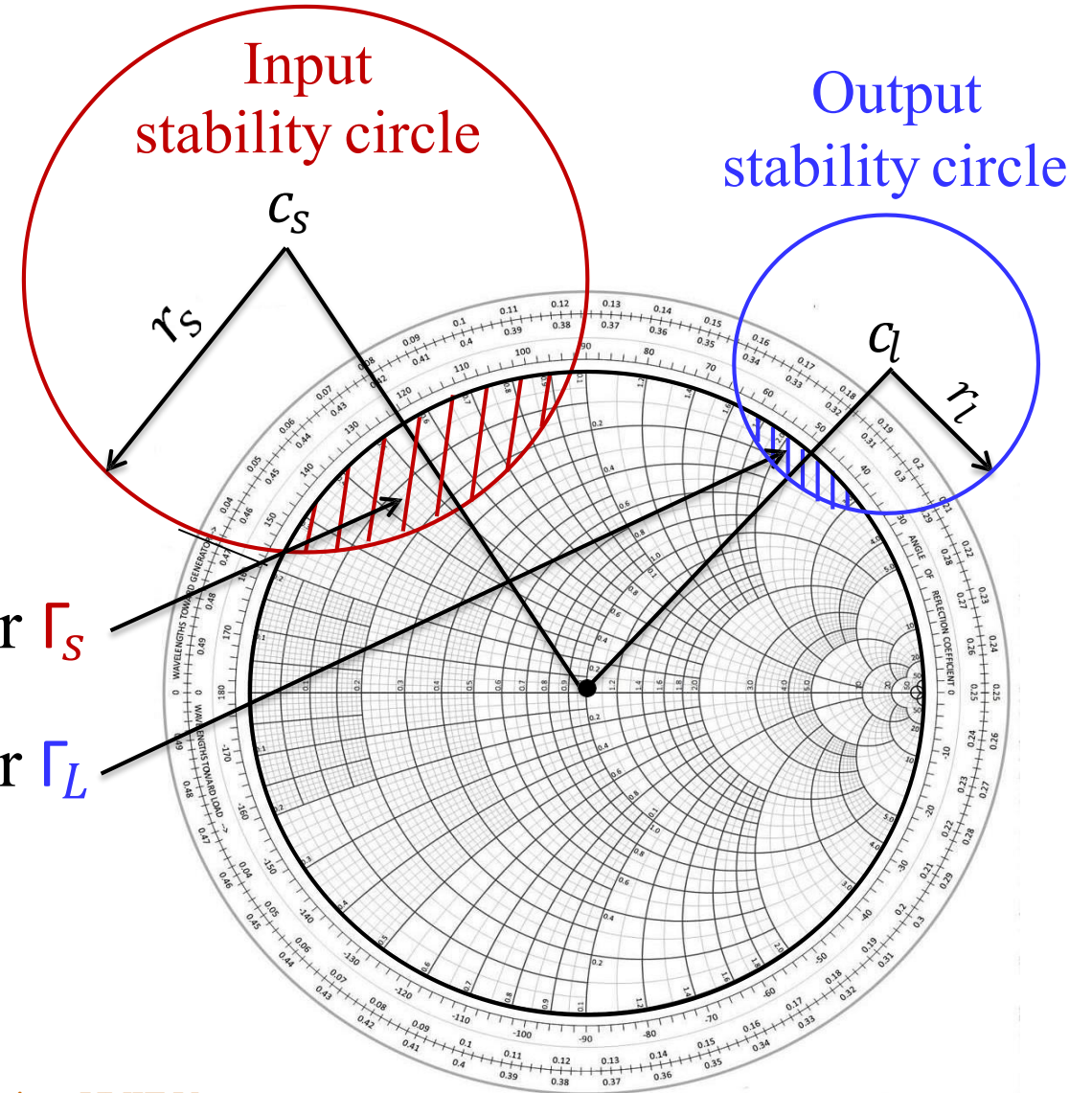

Constant Gain Circles: Unilateral Case

$$G_{tu} = \underbrace{\frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2}}_{g_s} |S_{21}|^2 \underbrace{\frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}}_{g_l}$$

$$G_{tu \max} = \underbrace{\frac{1}{1 - |S_{11}|^2}}_{g_{s \max}} |S_{21}|^2 \underbrace{\frac{1}{1 - |S_{22}|^2}}_{g_{l \max}}$$

For desired G_{tu} gain
choose g_s and g_l

$$\text{Normalized } g_s = g_{ns} = \frac{g_s}{g_{s \max}}$$

$$g_{ns} = \frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} (1 - |S_{11}|^2)$$

Constant Gain Circles: Unilateral Case (Contd.)

Solving for Γ_s in $|\Gamma_s - c_{gs}|^2 = r_{gs}^2$

$$c_{gs} = \frac{g_{ns} S_{11}^*}{1 - |S_{11}|^2 (1 - g_{ns})}$$
$$r_{gs} = \frac{\sqrt{1 - g_{ns}} (1 - |S_{11}|^2)}{1 - |S_{11}|^2 (1 - g_{ns})}$$

Center and radius of constant gain circle for Source

Similarly for Load

$$c_{gl} = \frac{g_{nl} S_{22}^*}{1 - |S_{22}|^2 (1 - g_{nl})}$$
$$r_{gl} = \frac{\sqrt{1 - g_{nl}} (1 - |S_{22}|^2)}{1 - |S_{22}|^2 (1 - g_{nl})}$$

Center and radius of constant gain circle for Load

For maximum gain, $g_{ns} = 1 \Rightarrow c_{gs} = S_{11}^* \quad r_{gs} = 0$

Unilateral Figure of Merit

Error when $|S_{12}| \neq 0$, but is very small and is assumed to be zero

$$\frac{G_t}{G_{tu}} = \frac{\frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_{out}\Gamma_L|^2}}{\frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}} = \frac{|1 - S_{22}\Gamma_L|^2}{|1 - \Gamma_{out}\Gamma_L|^2}$$

$$\frac{G_t}{G_{tu}} = \frac{|1 - S_{22}\Gamma_L|^2}{|1 - (S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s})\Gamma_L|^2} \quad \leftarrow \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_s}{1 - S_{11}\Gamma_s}$$

$$\begin{aligned} &= \frac{1}{\left| 1 - \frac{S_{12}S_{21}\Gamma_s\Gamma_L}{(1 - S_{11}\Gamma_s)(1 - S_{22}\Gamma_L)} \right|^2} \\ &= \frac{1}{|1 - X|^2} \end{aligned}$$

$$\frac{1}{(1 + |X|)^2} < \frac{G_t}{G_{tu}} < \frac{1}{(1 - |X|)^2}$$

Unilateral Figure of Merit (contd.)

When $\Gamma_s = S_{11}^*$ & $\Gamma_L = S_{22}^*$ $G_{tu} \longrightarrow G_{tu\ max}$

Maximum error introduced when using $G_{tu\ max}$ is bounded by

$$\frac{1}{(1 + M)^2} < \frac{G_t}{G_{tu\ max}} < \frac{1}{(1 - M)^2}$$

$$M = \frac{|S_{12}||S_{21}||S_{11}||S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

Unilateral Figure of Merit M should be less than 0.05

Design of an Amplifier

S-parameters of a GaAs MESFET at 8 GHz biased at $V_{ds} = 3\text{ V}$ and $I_{ds} = 30\text{ mA}$ with a $50\ \Omega$ reference are:

Design an amplifier for Gain = 10 dB.

$$S_{11} = 0.52 \angle -145^\circ$$

$$S_{12} = 0.03 \angle 20^\circ$$

$$S_{21} = 2.56 \angle 170^\circ$$

$$S_{22} = 0.48 \angle -20^\circ$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 0.168 \angle 197^\circ < 1$$

$$K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2 |S_{12}S_{21}|} = 3.53 > 1$$

Amplifier is
unconditionally stable

$$G_{tm} = |S_{21}|^2 = 6.55 = 8.16\text{ dB}$$

$$G_{tu\text{ max}} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2} = 11.67 = 10.67\text{ dB}$$

Design of an Amplifier (Contd.)

Maximum Gain Error:

$$M = \frac{|S_{12}||S_{21}||S_{11}||S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} = 0.04$$

$$\frac{1}{(1 + M)^2} < \frac{G_t}{G_{tu\ max}} < \frac{1}{(1 - M)^2}$$

$$0.92 < \frac{G_t}{G_{tu\ max}} < 1.09$$

$$-0.36\ dB < \frac{G_t}{G_{tu\ max}} < +0.37\ dB$$

Design of an Amplifier (Contd.)

$$G_{tu \max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$
$$= \underset{\substack{\downarrow \\ g_{smax}}}{1.37} \times 6.55 \times \underset{\substack{\downarrow \\ g_{lmax}}}{1.3} = 11.67 = 10.67 \text{ dB}$$

Design of an amplifier for Gain = 10 dB = 10

Choose $g_s \leq g_{smax}$

Let $g_s = 1.25$, then $g_l = 10 / (1.25 \times 6.55) = 1.22$

$$g_{ns} = g_s (1 - |S_{11}|^2) = 1.25 \times (1 - 0.52^2) = 0.91$$

$$g_{nl} = g_l (1 - |S_{22}|^2) = 1.22 \times (1 - 0.48^2) = 0.94$$

Design of an Amplifier (Contd.)

Calculate center and radius of constant gain circles:

$$c_{gs} = \frac{g_{ns} S_{11}^*}{1 - |S_{11}|^2 (1 - g_{ns})} = 0.485 / \underline{145^\circ}$$

$$r_{gs} = \frac{\sqrt{1 - g_{ns}} (1 - |S_{11}|^2)}{1 - |S_{11}|^2 (1 - g_{ns})} = 0.224$$

$$c_{gl} = \frac{g_{nl} S_{22}^*}{1 - |S_{22}|^2 (1 - g_{nl})} = 0.457 / \underline{20^\circ}$$

$$r_{gl} = \frac{\sqrt{1 - g_{nl}} (1 - |S_{22}|^2)}{1 - |S_{22}|^2 (1 - g_{nl})} = 0.19$$

Design of an Amplifier (Γ_s and Γ_L selection)


$$c_{gs} = 0.485 \angle 145^\circ, r_{gs} = 0.224$$

$$c_{gl} = 0.457 \angle 20^\circ, r_{gl} = 0.19$$

Since the transistor is unconditionally stable, any point on the constant gain circles can be chosen for Γ_s and Γ_L



$$\text{Chosen: } \Gamma_s = 0.261 \angle 145^\circ$$
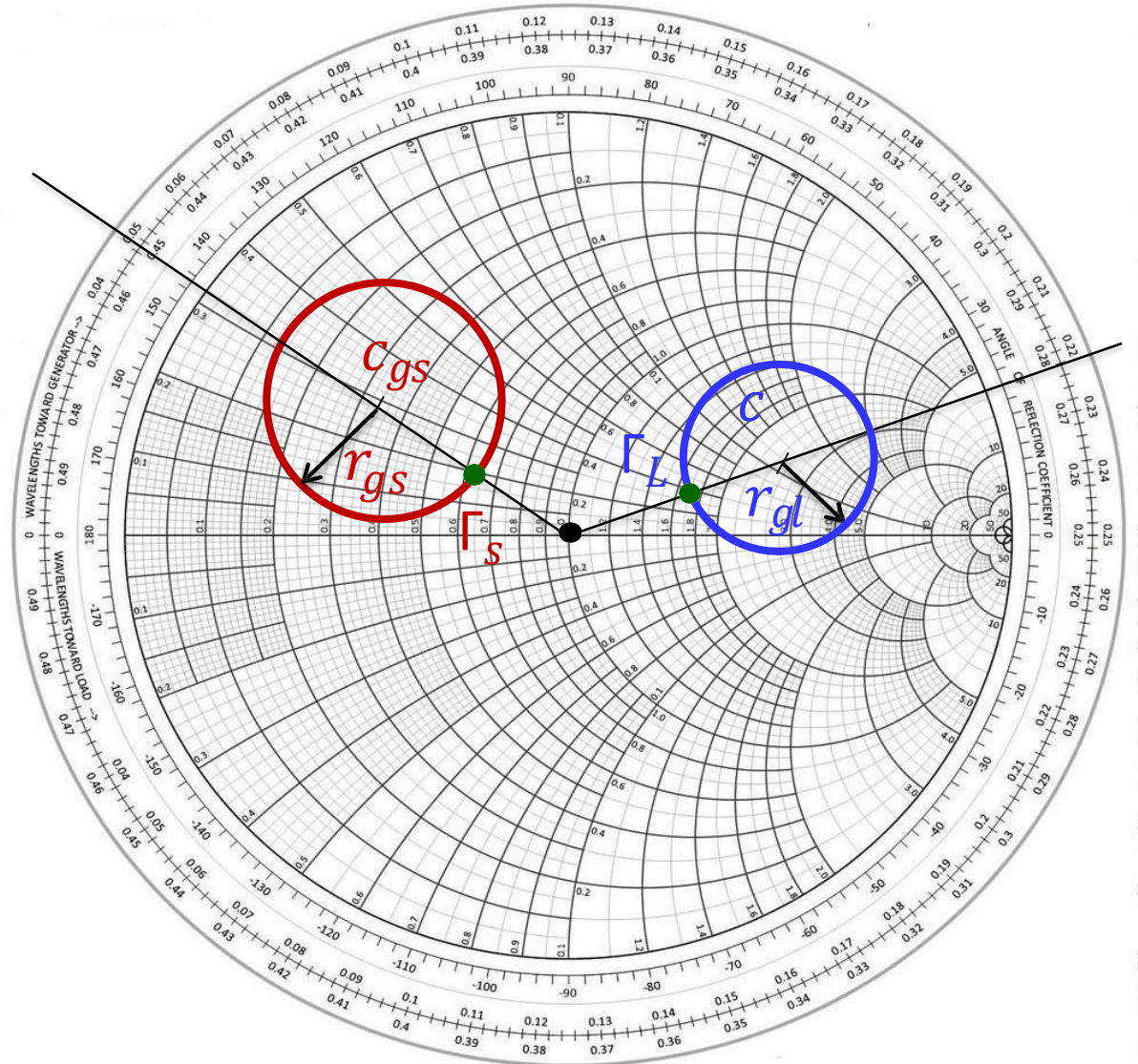
$$\text{Chosen: } \Gamma_L = 0.267 \angle 20^\circ$$





Design of an Amplifier (IMN for Γ_s)

$$\Gamma_s = 0.261 \angle 145^\circ$$

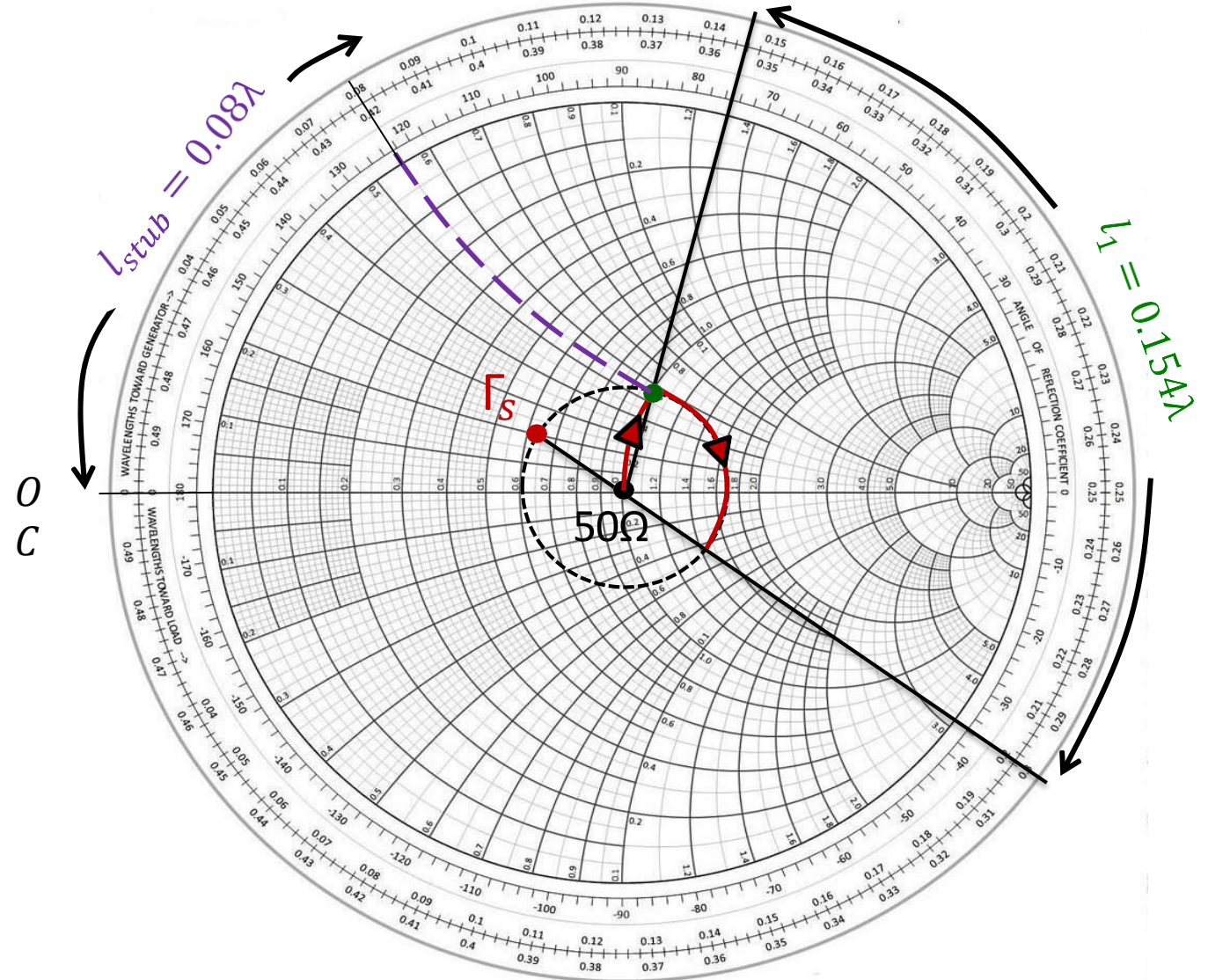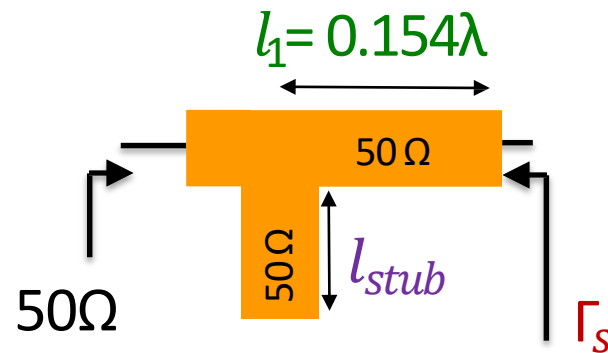


Design of an Amplifier (IMN for Γ_L)

$$\Gamma_L = 0.267 \angle 20^\circ$$

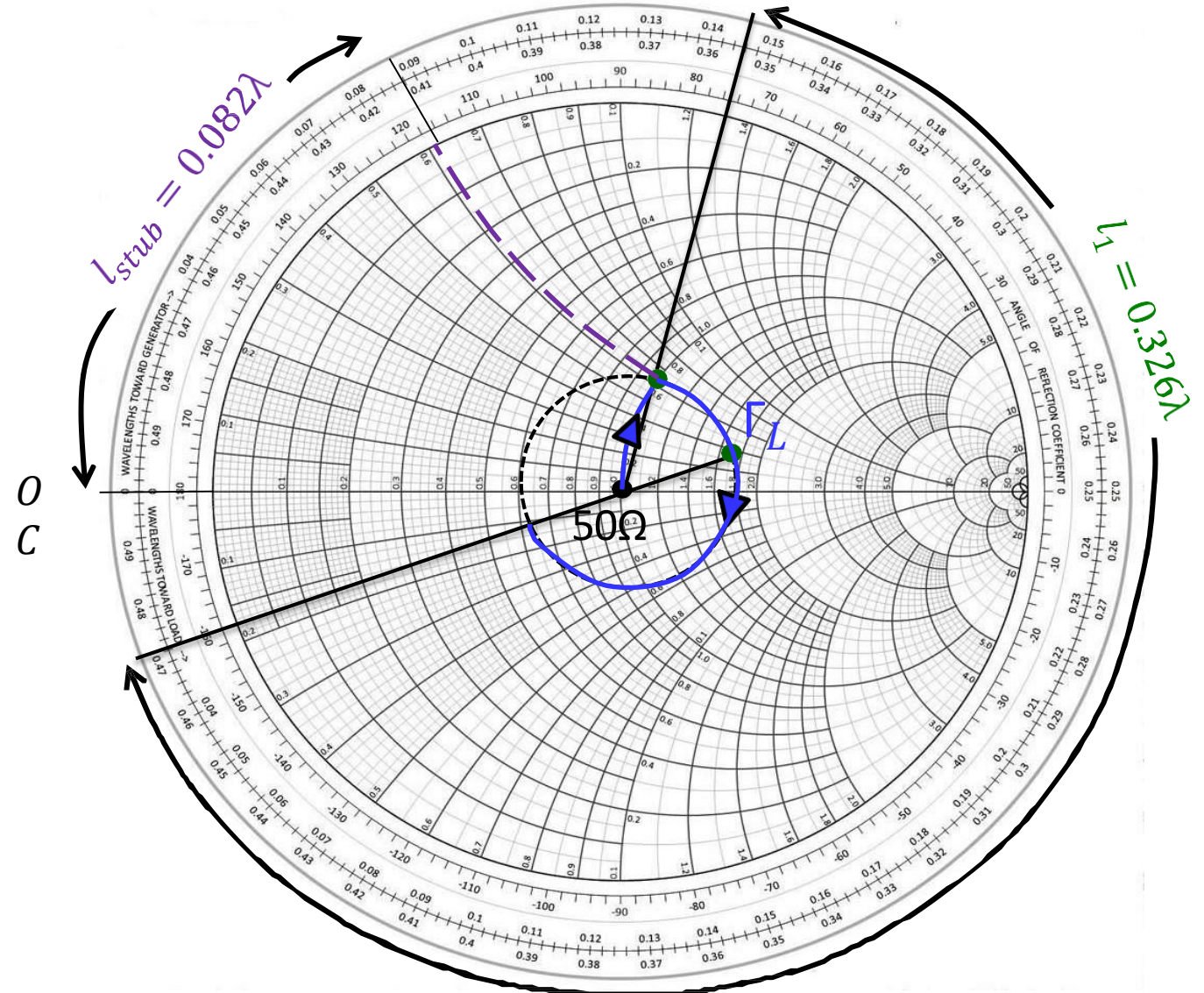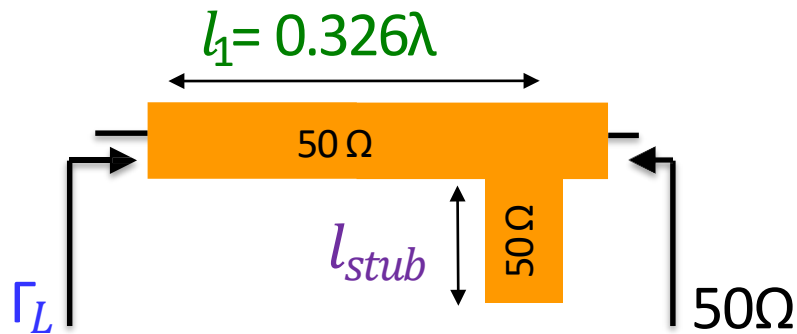

Design of an Amplifier (Final Circuit)

Final Amplifier Circuit Diagram

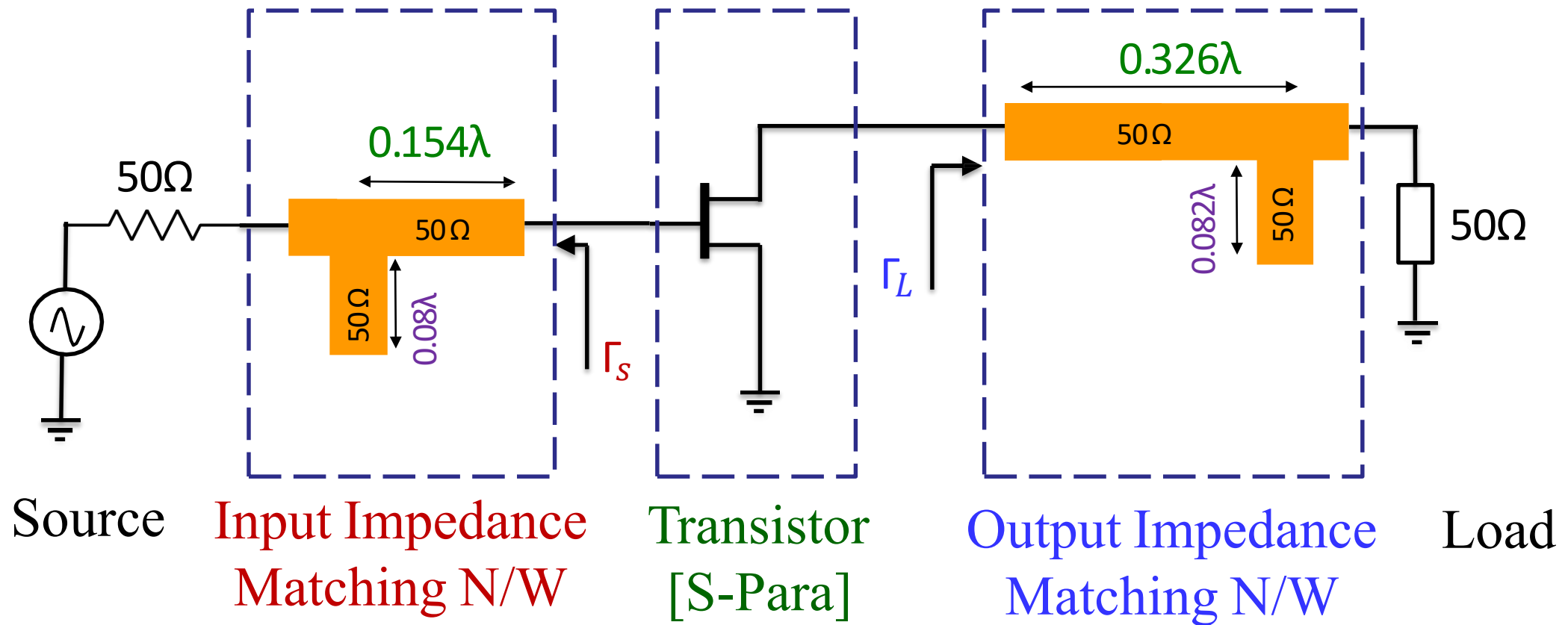



Noise figure.

- Noise figure F is defined as “the ratio of the input SNR to the output SNR”.

$$F = \text{Input SNR} / \text{Output SNR}$$



THANKYOU